

Solar Power

Noji Ratzlaff

KNØJI


noji.com/hamradio

Many applications

Used everywhere there's sun

Becoming more universal

Becoming less expensive

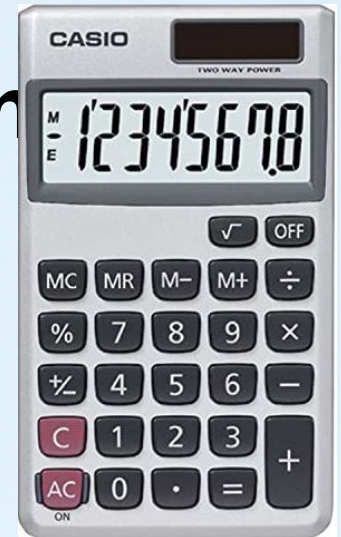


Requires three components

Solar panel

Charge controller

Rechargeable battery

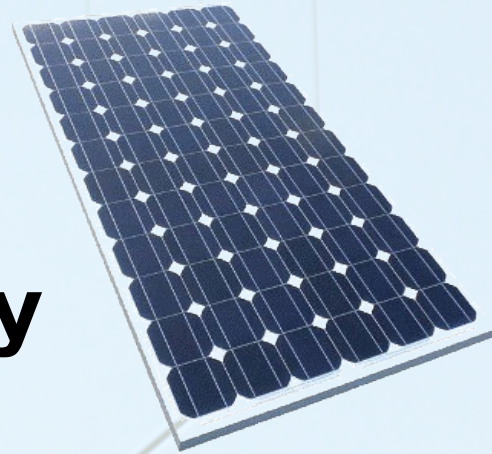

Solar cell types

Silicon - about 16% efficient

Most common on homes, inexpensive

Polycrystalline - about 18% efficient

Common on homes, more expensive

Monocrystalline - about 23% efficient

Becoming more common, most expensive

Thin film - about 13% efficient

Small appliances, least expensive

**(phone charger, small lights, calculators,
etc.)**

Your charge controller is key

Regulates the voltage

Controls the current

Adjusts to the battery type

Can run 24/7

PWM or MPPT


***Never connect a panel to a battery
without one***

***Do not connect charge controllers
to each other***

PWM charge controller

Less expensive

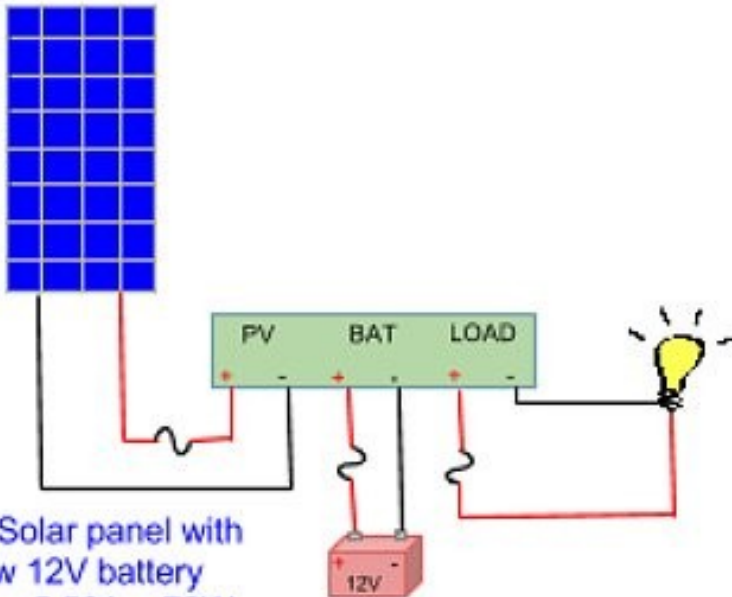12V Solar panel potential
 $18V \times 5.56A = 100W$




12V Solar panel with
low 12V battery
 $13V \times 5.56A = 72W$

12V Solar Panel with PWM charge controller
charging a low 12V battery

28% loss

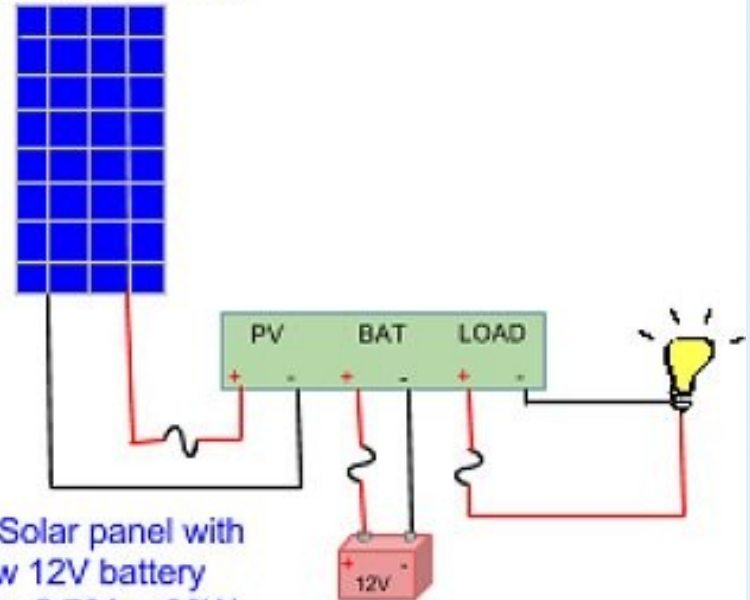24V Solar panel potential
 $36V \times 2.78A = 100W$



24V Solar panel with
low 12V battery
 $13V \times 2.78A = 36W$

24V solar panel with PWM charge controller
charging a low 12V battery


64% loss

MPPT charge controller

More efficient

12V Solar panel potential

$$18V \times 5.56A = 100W$$

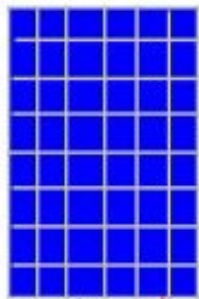

$$18V \div 13V \times 5.56A = 7.7A \text{ output}$$




12V Solar panel with
low 12V battery
 $13V \times 7.7A = 100W$

12V Solar Panel with MPPT charge controller
charging a low 12V battery

Virtually no loss

Three 20V Solar panels in series for 60V

$$3 \times 30.5V \times 8.19A = 750W$$

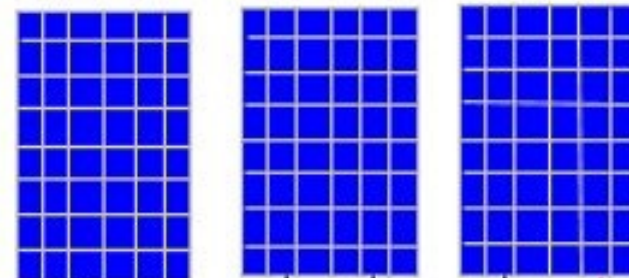

$$30.5V \times 3 \div 52V \times 8.19A = 14.41A \text{ output}$$

3x 20V Solar panel with
low 48V battery
 $52V \times 14.41A = 750W$

Three 20V Solar Panels in series with MPPT
charge controller charging a low 48V battery

Virtually no loss

Load the controller

It's best to apply the load to the controller

It's ok to apply the load to the battery

Do not apply



Battery type

Use a deep-cycle battery, if available

Today's battery types include

- **SLA**
- **AGM**
- **Li-Ion**
- **LiPo**
- **LiFePO₄**



Battery practices to avoid

Do not connect batteries together

- **of different nominal voltages (12 V / 24 V)**
- **of different types (AGM / SLA / LiFePO₄)**
- **of different capacities (Ah)**

Do not leave batteries charging forever

- **unless you're using a smart charger**

Do not dispose of batteries in your trash

Do not keep batteries that show any signs of leaking or bloating

Connectors

Many solar panels come with MC4 connectors

I tend to convert them all to Andersons



Anderson to MC4

Put it all together



Multiple panels

Can connect them in parallel if they have the same output voltage, to increase wattage

Can connect them in series, to increase voltage

Try and connect *identical panels* together; different (wattage, chemistry) types *can* work together, if you know what you're doing (similar open-circuit

Just how much do you need?

Yaesu FT-857D (maximum 23 A, but only being used at 50% duty cycle) = 11.5 A (average)

LDG AT-100ProII tuner = 0.5 A

Laptop (charger and inverter) = 6.6 A

LED light stick (for nighttime work) = 0.2 A

Total draw = $11.5 + 0.5 + 6.6 + 0.2 = 18.8$ A

You will need $18.8 \text{ A} \times 12 \text{ V} = 225.6 \text{ W}$

Energy required for one hour = 225.6 Wh

Your power calculation

Energy required for one hour = 225.6 Wh

Assuming a 75% solar (PWM) solution, you'll need a $225.6 \text{ Wh} \div 0.75 = 300 \text{ W}$ solar panel charging your battery for an hour

Or a **100-watt panel** charging for three hours

For three operating hours, you'll need a battery that can handle $18.8 \text{ A} \times 3 \text{ hours} = 56.4 \text{ Ah}$

But to keep the battery from draining too far, use a **100 Ah deep-cycle battery** to provide 56.4 Ah

Your charge controller needs to handle 18.8 A, so I recommend a **30 A controller**

Your shopping list

Basic needs, not including cabling

- **One 100 W solar panel**
- **One 100 Ah battery**
- **One 30 A PWM 12 V charge controller**

Alternatively,

- **Two 50 W solar panels**
- **Two 50 Ah batteries**
- **One 20 A MPPT 12 V charge controller**

Now, go have some fun

Will this work on a cloudy day?

- **Outdoors, yes; indoors, maybe not so much**

Where can I purchase these things?

- **Amazon smile (smile.amazon.com)**

Where can I dispose of old batteries?

- **Interstate Batteries, Batteries Plus**

How can I get rid of working solar panels?

- **Give them to Noji**